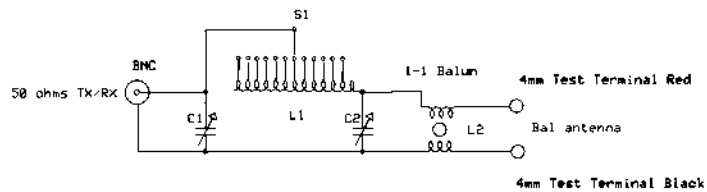


QRP A.T.U

Built at for my FT817. Works well with long wire and dipoles. Has a balanced input which is fed into pie network The inductor is multi tapped toroid . Will tune from 7mhz to 30mhz.



C1 & C2 Miniature Tuning Capacitor - AM Rapid Electronics Order Code: 12-0255

S1 1 POLE 12 WAY ROTARY SWITCH (RC) Rapid Electronics Order Code: 79-0100

L1 66t tapped at every 6t on T68-2 Toroid

L2 12t Bifilar wound on T58-2 Toroid

Toroids from www.sycocomp.co.uk

Works on Dipole Long wires 3ft to 66ft

Keep power to 5watts due to switch and capacitor ratings

| | |
|-------------|-----------------------|
| G8GRL | |
| ATU | |
| Kim Edwards | Rev 1.0 25/12/2010 |